

## WORD BANK:

CIRCUIT

CIRCLE

BATTERY

LIGHT BULB

BREAK

LIGHT

WRONG

CORRECT



Electricity moves in a path called a \_\_\_\_\_. Power from the battery moves through the wires, into the \_\_\_\_\_ and back again!

If there is a \_\_\_\_\_ in the circuit, the electricity cannot move and the light will not light up!

To take our quiz, try to match the correct answers. If you get the answers \_\_\_\_\_, the light bulb will turn on!

